

# Electrical oscillation with external excitation

Andreas Höschler  
Smartsoft GmbH


26 Jun 2015

# Contents

<b>1 Damped LC tank with external excitation</b>	<b>1</b>
1.1 Solving the homogeneous part of the differential equation . . . . .	1
1.2 Finding a particular solution for the inhomogeneous differential equation . . . . .	4
1.3 Combining the general and the particular solution . . . . .	6
1.4 Energy Consideration . . . . .	8
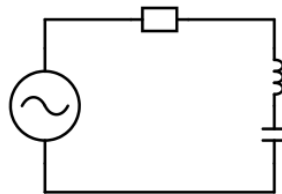
## 1 Damped LC tank with external excitation

We consider a resistor, an inductance and a cap in series excited by an external AC signal.



This circuit is mathematically described by

$$U_G = U_R + U_L + U_C \quad (1)$$

$$U_0 \sin(\eta t) = RI + LI' + \frac{1}{C}Q \quad (2)$$

$$Q'' + \frac{R}{L}Q' + \frac{1}{CL}Q = \frac{U_0}{L} \sin(\eta t) \quad (3)$$

### 1.1 Solving the homogeneous part of the differential equation

We solve the homogeneous part of the differential equation LINK first

$$Q'' + \frac{R}{L}Q' + \frac{1}{CL}Q = 0 \quad (4)$$

using the approach

$$\begin{aligned} Q &= Ke^{i\sigma t} \\ Q' &= Ki\sigma e^{i\sigma t} \\ Q'' &= -K\sigma^2 e^{i\sigma t} \end{aligned}$$

Substitution into the differential equation gives

$$\begin{aligned} -K\sigma^2 e^{i\sigma t} + \frac{R}{L} K i \sigma e^{i\sigma t} + \frac{1}{CL} K e^{i\sigma t} &= 0 \\ \left( \sigma^2 - \frac{R}{L} i \sigma - \frac{1}{CL} \right) K e^{i\sigma t} &= 0 \end{aligned}$$

This equation is true for all  $t$  only if

$$\sigma^2 - \frac{R}{L} i \sigma - \frac{1}{CL} = 0$$

is true. We solve this as follows:

$$\begin{aligned} p &= -\frac{R}{L} i \\ q &= -\frac{1}{CL} \end{aligned}$$

$$\begin{aligned} \sigma_1 &= -\frac{p}{2} + \sqrt{\left(\frac{p}{2}\right)^2 - q} \\ \sigma_2 &= -\frac{p}{2} - \sqrt{\left(\frac{p}{2}\right)^2 - q} \end{aligned}$$

$$\begin{aligned} \sigma_1 &= -\frac{-\frac{R}{L} i}{2} + \sqrt{\left(\frac{-\frac{R}{L} i}{2}\right)^2 - \left(-\frac{1}{CL}\right)} \\ \sigma_1 &= \frac{R}{2L} i + \sqrt{-\left(\frac{R}{2L}\right)^2 + \frac{1}{CL}} \\ \sigma_2 &= \frac{R}{2L} i - \sqrt{-\left(\frac{R}{2L}\right)^2 + \frac{1}{CL}} \end{aligned}$$

We define

$$\omega = \sqrt{-\left(\frac{R}{2L}\right)^2 + \frac{1}{CL}}$$

and thus get the following two solutions:

$$\begin{aligned} Q &= K e^{i\sigma_1 t} \\ Q &= K e^{i\left(\frac{R}{2L} i + \omega\right) t} \\ Q &= K e^{-\frac{R}{2L} t} e^{i\omega t} \\ Q &= K e^{-\frac{R}{2L} t} (\cos(\omega t) + i \sin(\omega t)) \end{aligned}$$

$$\begin{aligned}
Q &= Ke^{i\sigma_2 t} \\
Q &= Ke^{i\left(\frac{R}{2L}i - \omega\right)t} \\
Q &= Ke^{-\frac{R}{2L}t} e^{-i\omega t} \\
Q &= Ke^{-\frac{R}{2L}t} (\cos(\omega t) - i \sin(\omega t))
\end{aligned}$$

The general solution for the homogeneous differential equation can therefore be written as

$$\begin{aligned}
Q &= Ae^{-\frac{R}{2L}t} (\cos(\omega t) + i \sin(\omega t)) + Be^{-\frac{R}{2L}t} (\cos(\omega t) - i \sin(\omega t)) \\
Q &= e^{-\frac{R}{2L}t} (A \cos(\omega t) + Ai \sin(\omega t)) + e^{-\frac{R}{2L}t} (B \cos(\omega t) - Bi \sin(\omega t)) \\
Q &= e^{-\frac{R}{2L}t} (A \cos(\omega t) + Ai \sin(\omega t) + B \cos(\omega t) - Bi \sin(\omega t)) \\
Q &= e^{-\frac{R}{2L}t} ((A + B) \cos(\omega t) + i(A - B) \sin(\omega t))
\end{aligned}$$

or after replacing the factors

$$Q = e^{-\frac{R}{2L}t} (K_1 \cos(\omega t) + iK_2 \sin(\omega t))$$

Since the differential equation is linear we can rewrite this as follows

$$Q = e^{-\frac{R}{2L}t} (K_1 \cos(\omega t) + K_2 \sin(\omega t))$$

or even shorter like so

$$Q = e^{-\frac{R}{2L}t} K \sin(\omega t + \varphi) \quad (5)$$

$$\omega = \sqrt{\omega_0^2 - \rho^2} \quad (6)$$

$$\omega_0^2 = \frac{1}{CL} \quad (7)$$

$$\rho = \frac{R}{2L} \quad (8)$$

with the two freely choosable constants  $K$  und  $\varphi$ . Please note the dependence of the resonance frequency from the resistance.

$$f(R) = \frac{1}{2\pi} \sqrt{-\left(\frac{R}{2L}\right)^2 + \frac{1}{CL}} \quad (9)$$

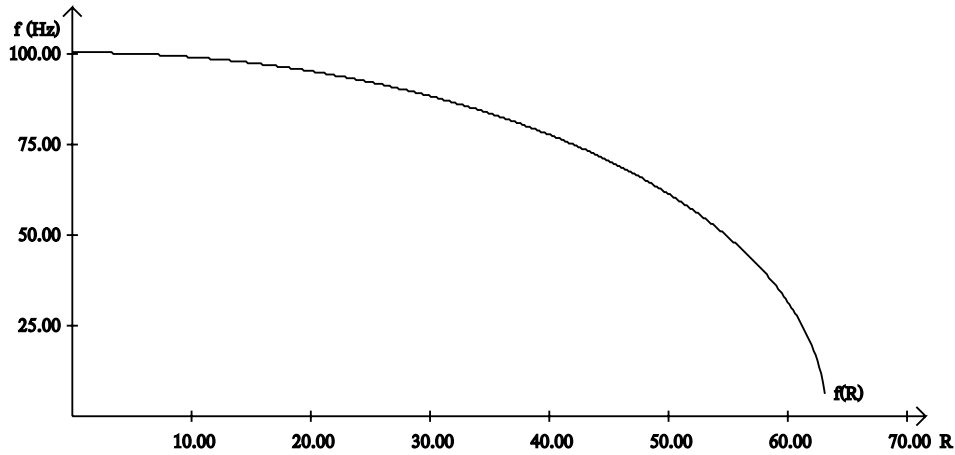


Figure 1:  $C=50E-6$ ;  $L=50E-3$

## 1.2 Finding a particular solution for the inhomogeneous differential equation

We find a particular solution for the inhomogeneous differential equation by trying a suitable approach.

$$Q'' + \frac{R}{L}Q' + \frac{1}{CL}Q = \frac{U_0}{L} \sin(\eta t)$$

A suitable approach for the above equation is

$$\begin{aligned} Q(t) &= De^{i(\eta t + \delta)} \\ Q'(t) &= Di\eta e^{i(\eta t + \delta)} \\ Q''(t) &= -D\eta^2 e^{i(\eta t + \delta)} \end{aligned}$$

Substituted into the differential equation we get

$$\begin{aligned} Q''(t) + \frac{R}{L}Q'(t) + \frac{1}{CL}Q(t) &= \frac{U_0}{L}e^{i\eta t} \\ -D\eta^2 e^{i(\eta t + \delta)} + \frac{R}{L}Di\eta e^{i(\eta t + \delta)} + \frac{1}{CL}De^{i(\eta t + \delta)} &= \frac{U_0}{L}e^{i\eta t} \\ De^{i(\eta t + \delta)} \left( \frac{R}{L}i\eta + \frac{1}{CL} - \eta^2 \right) &= \frac{U_0}{L}e^{i\eta t} \\ De^{i\delta} \left( \frac{R}{L}i\eta + \frac{1}{CL} - \eta^2 \right) &= \frac{U_0}{L} \end{aligned}$$

$$\begin{aligned}
De^{i\delta} &= \frac{U_0}{L \left( \frac{1}{CL} - \eta^2 + \frac{R}{L}i\eta \right)} \\
De^{i\delta} &= \frac{U_0 \left( \frac{1}{CL} - \eta^2 - \frac{R}{L}i\eta \right)}{L \left( \frac{1}{CL} - \eta^2 + \frac{R}{L}i\eta \right) \left( \frac{1}{CL} - \eta^2 - \frac{R}{L}i\eta \right)} \\
De^{i\delta} &= \frac{U_0 \left( \frac{1}{CL} - \eta^2 - \frac{R}{L}i\eta \right)}{L \left( \left( \frac{1}{CL} - \eta^2 \right)^2 + \left( \frac{R}{L}\eta \right)^2 \right)} \\
De^{i\delta} &= \frac{U_0}{L \left( \left( \frac{1}{CL} - \eta^2 \right)^2 + \left( \frac{R}{L}\eta \right)^2 \right)} \left( \frac{1}{CL} - \eta^2 - \frac{R}{L}i\eta \right)
\end{aligned}$$

The value  $D$  is the length of the complex number on the right.

$$\begin{aligned}
D &= \frac{U_0}{L \left( \left( \frac{1}{CL} - \eta^2 \right)^2 + \left( \frac{R}{L}\eta \right)^2 \right)} \sqrt{\left( \frac{1}{CL} - \eta^2 \right)^2 + \left( \frac{R}{L}\eta \right)^2} \\
D &= \frac{U_0}{L \sqrt{\left( \frac{1}{CL} - \eta^2 \right)^2 + \left( \frac{R}{L}\eta \right)^2}}
\end{aligned}$$

The angle  $\delta$  is determined as follows:

$$\begin{aligned}
\tan \delta &= \frac{D_I}{D_R} \\
\sin \delta &= \frac{D_I}{D} \\
\cos \delta &= \frac{D_R}{D}
\end{aligned}$$

$$\begin{aligned}
D_R &= \frac{U_0 \left( \frac{1}{CL} - \eta^2 \right)}{L \left( \left( \frac{1}{CL} - \eta^2 \right)^2 + \left( \frac{R}{L}\eta \right)^2 \right)} \\
D_I &= -\frac{U_0 \left( \frac{R}{L}\eta \right)}{L \left( \left( \frac{1}{CL} - \eta^2 \right)^2 + \left( \frac{R}{L}\eta \right)^2 \right)} \\
D &= \frac{U_0}{L \sqrt{\left( \frac{1}{CL} - \eta^2 \right)^2 + \left( \frac{R}{L}\eta \right)^2}}
\end{aligned}$$

$$\begin{aligned}
\tan \delta &= -\frac{R\eta}{L \left( \frac{1}{CL} - \eta^2 \right)} \\
\sin \delta &= -\frac{R}{L}\eta \\
\cos \delta &= \frac{1}{CL} - \eta^2
\end{aligned}$$

$$Q(t) = D \sin(\eta t + \delta)$$

### 1.3 Combining the general and the particular solution

We combine the general solution for the homogeneous differential equation

$$\begin{aligned} Q &= e^{-\frac{R}{2L}t} K \sin(\omega t + \varphi) \\ \omega &= \sqrt{\omega_0^2 - \rho^2} \\ \omega_0 &= \sqrt{\frac{1}{CL}} \\ \rho &= \frac{R}{2L} \end{aligned}$$

and the particular solution of the inhomogeneous differential equation

$$\begin{aligned} Q(t) &= D \sin(\eta t + \delta) \\ D &= \frac{U_0}{L \sqrt{\left(\frac{1}{CL} - \eta^2\right)^2 + \left(\frac{R}{L}\eta\right)^2}} \\ \tan \delta &= -\frac{R\eta}{L \left(\frac{1}{CL} - \eta^2\right)} \end{aligned}$$

into a total solution by summation:

$$Q(t) = e^{-\frac{R}{2L}t} K \sin(\omega t + \varphi) + D \sin(\eta t + \delta) \quad (10)$$

Since the e-Function approaches 0 for large values of  $t$  only the particular solution remains after an initiation period.

$$Q(t) = D \sin(\eta t + \delta) \quad (11)$$

We divide by  $C$  to get the voltage in the cap, take first derivatives to get the current and take the second derivative to get the voltage over the coil.

$$\begin{aligned} Q(t) &= D \sin(\eta t + \delta) \\ Q'(t) &= D\eta \cos(\eta t + \delta) \\ Q''(t) &= -D\eta^2 \sin(\eta t + \delta) \\ U_C(t) &= \frac{Q(t)}{C} \\ U_L(t) &= LQ''(t) \\ I(t) &= Q'(t) \\ \delta &= \arctan\left(-\frac{R\eta}{L \left(\frac{1}{CL} - \eta^2\right)}\right) \end{aligned}$$

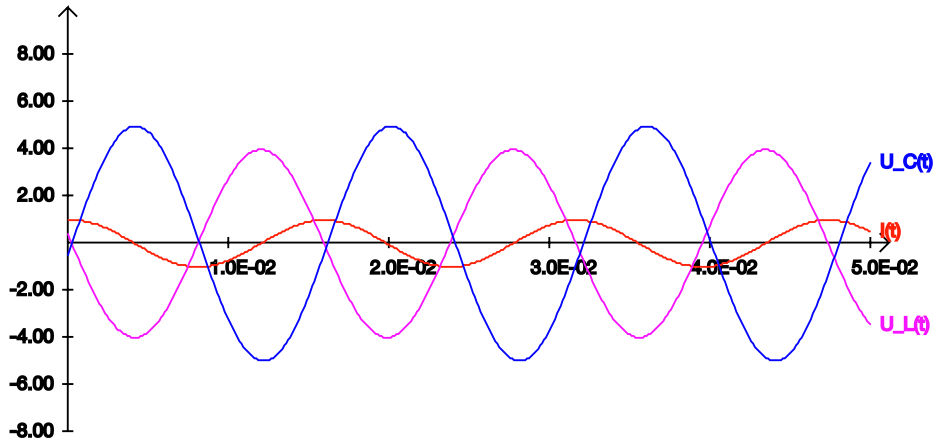


Figure 2:  $C=50E-6$ ;  $L=100E-3$ ;  $R=1$ ;  $U_0=1$ ;  $\eta=400$ ; Factor  $I(t)$ : 10.00

We determine the peak voltage in the cap and the peak current with respect to  $f$  (resonance frequency):

$$\begin{aligned}
 Q(t) &= D \sin(\eta t + \delta) \\
 U_s(f) &= \frac{D}{C} \\
 U_s(f) &= \frac{U_0}{LC \sqrt{\left(\frac{1}{CL} - \eta^2\right)^2 + \left(\frac{R}{L}\eta\right)^2}} \\
 U_s(f) &= \frac{U_0}{LC \sqrt{\left(\frac{1}{CL} - (2\pi f)^2\right)^2 + \left(2\pi f \frac{R}{L}\right)^2}}
 \end{aligned}$$

$$\begin{aligned}
 I(t) &= D\eta \cos(\eta t + \delta) \\
 I_s(f) &= D\eta \\
 I_s(f) &= \frac{U_0}{L \sqrt{\left(\frac{1}{CL} - \eta^2\right)^2 + \left(\frac{R}{L}\eta\right)^2}} \eta \\
 I_s(f) &= \frac{2\pi f U_0}{L \sqrt{\left(\frac{1}{CL} - (2\pi f)^2\right)^2 + \left(2\pi f \frac{R}{L}\right)^2}}
 \end{aligned}$$



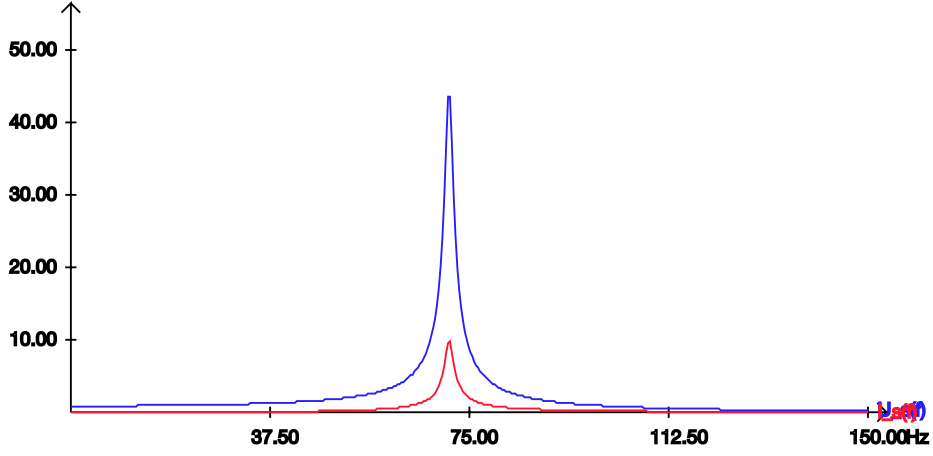


Figure 3:  $C=50E-6$ ;  $L=100E-3$ ;  $R=1$ ;  $U_0=1$ ; Factor  $L_s(f)$ : 10.00

If we excite the series tank with its resonance frequency we get high voltages over the components and a very high current only limited by the resistance of the wire.

## 1.4 Energy Consideration

The power going into the circuit is given by

$$\begin{aligned}
 P &= \frac{1}{T} \int_0^T U_G(t) I(t) dt \\
 P &= \frac{1}{T} \int_0^T U_0 \sin(\eta t) D \eta \cos(\eta t + \delta) dt \\
 P &= \frac{U_0 D \eta}{T} \int_0^T \sin(\eta t) \cos(\eta t + \delta) dt \\
 P &= \frac{U_0 D \eta}{T} \left[ -\frac{2\eta t \sin \delta + \cos(2\eta t + \delta)}{4\eta} \right]_0^T \\
 P &= \frac{U_0 D \eta}{T} \left( -\frac{2\eta T \sin \delta + \cos(2\eta T + \delta)}{4\eta} - \left( -\frac{\cos \delta}{4\eta} \right) \right) \\
 P &= \frac{U_0 D}{4T} (\cos \delta - 2\eta T \sin \delta - \cos(2\eta T + \delta)) \\
 \eta &= \frac{2\pi}{T} \\
 T &= \frac{2\pi}{\eta}
 \end{aligned}$$

$$P = \frac{U_0 D}{4 \frac{2\pi}{\eta}} \left( \cos \delta - 2\eta \frac{2\pi}{\eta} \sin \delta - \cos \left( 2\eta \frac{2\pi}{\eta} + \delta \right) \right)$$

This gets us the following expression for the input power.

$$P_{in} = \frac{U_0 D \eta}{8\pi} (\cos \delta - 4\pi \sin \delta - \cos(4\pi + \delta)) \quad (12)$$

$$\delta = \arctan \left( -\frac{R\eta}{L \left( \frac{1}{CL} - \eta^2 \right)} \right) \quad (13)$$

$$D = \frac{U_0}{L \sqrt{\left( \frac{1}{CL} - \eta^2 \right)^2 + \left( \frac{R}{L} \eta \right)^2}} \quad (14)$$

The circulating power in the circuit is defined as

$$P_{circ}(t) = \frac{d(W(t))}{dt}$$

with

$$W(t) = \frac{1}{2} C (U_C(t))^2 + \frac{1}{2} L (I(t))^2$$

$$\begin{aligned} U_C(t) &= \frac{D}{C} \sin(\eta t + \delta) \\ I(t) &= D\eta \cos(\eta t + \delta) \end{aligned}$$

$$\begin{aligned}
P_{circ}(t) &= \frac{d(W(t))}{dt} \\
P_{circ}(t) &= \frac{d\left(\frac{1}{2}C(U_C(t))^2 + \frac{1}{2}L(I(t))^2\right)}{dt} \\
P_{circ}(t) &= \frac{d\left(\frac{1}{2}C\left(\frac{D}{C}\sin(\eta t + \delta)\right)^2 + \frac{1}{2}L(D\eta\cos(\eta t + \delta))^2\right)}{dt} \\
P_{circ}(t) &= \frac{1}{2}C\frac{d\left(\left(\frac{D}{C}\sin(\eta t + \delta)\right)^2\right)}{dt} + \frac{1}{2}L\frac{d\left(\left(D\eta\cos(\eta t + \delta)\right)^2\right)}{dt} \\
P_{circ}(t) &= C\frac{D}{C}\left(\eta\frac{dt}{dt} + 0\right)\cos(\eta t + \delta)\left(\frac{D}{C}\sin(\eta t + \delta)\right) - LD\eta\left(\eta\frac{dt}{dt} + 0\right)\sin(\eta t + \delta)(D\eta\cos(\eta t + \delta)) \\
P_{circ}(t) &= C\frac{D}{C}\eta\cos(\eta t + \delta)\frac{D}{C}\sin(\eta t + \delta) - LD\eta^2\sin(\eta t + \delta)D\eta\cos(\eta t + \delta) \\
P_{circ}(t) &= D\eta\cos(\eta t + \delta)\frac{D}{C}\sin(\eta t + \delta) - LD\eta^2\sin(\eta t + \delta)D\eta\cos(\eta t + \delta) \\
P_{circ}(t) &= D\eta\frac{D}{C}\cos(\eta t + \delta)\sin(\eta t + \delta) - LD\eta^2D\eta\sin(\eta t + \delta)\cos(\eta t + \delta) \\
P_{circ}(t) &= \left(D\eta\frac{D}{C} - LD\eta^2D\eta\right)\cos(\eta t + \delta)\sin(\eta t + \delta) \\
P_{circ}(t) &= D^2\left(\eta\frac{1}{C} - L\eta^2\eta\right)\cos(\eta t + \delta)\sin(\eta t + \delta) \\
P_{circ}(t) &= D^2\eta\left(\frac{1}{C} - L\eta^2\right)\cos(\eta t + \delta)\sin(\eta t + \delta) \\
D &= \frac{U_0}{L\sqrt{\left(\frac{1}{CL} - \eta^2\right)^2 + \left(\frac{R}{L}\eta\right)^2}} \\
\delta &= \arctan\left(-\frac{R\eta}{L\left(\frac{1}{CL} - \eta^2\right)}\right)
\end{aligned}$$

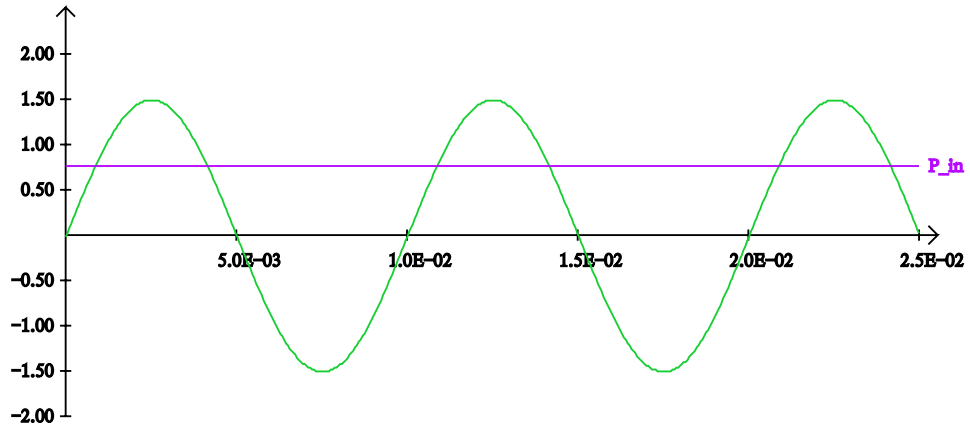


Figure 4:  $C=50E-6$ ;  $L=50E-3$ ;  $R=0.25$ ;  $U_0=12$ ;  $\eta=314$ ; Factor  $P_{in}$ : 100.00

We have scaled  $P_{in}$  with a factor of 100 in the figure above. The Input power is very small compared to the circulating power for  $R = 0.25\text{Ohm}$ .